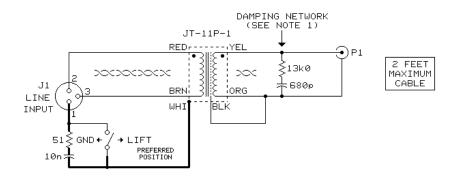
JT-11P-1 BALANCED XLR INPUT TO UNBALANCED RCA OUTPUT



NOTES:

- 1. THE DAMPING NETWORK SHOWN IS NECESSARY IF THE IMPEDANCE OF THE UNBALANCED INPUT IS OVER 10 k Ω , WHICH IS TYPICAL. OMIT NETWORK ONLY IF INPUT IMPEDANCE IS EXACTLY 10 k Ω .
- 2. FOR BEST TRANSIENT RESPONSE, KEEP SECONDARY LOAD CAPACITANCE UNDER 100 pF. (ABOUT 2 FEET OF TYPICAL CABLE CONNECTED TO P1)
- 3. PRIMARY (RED/BRN) AND SECONDARY (YEL/ORG) LEADS SHOULD BE TWISTED AS SHOWN AND WIRING SHOWN AS THICK LINE SHOULD BE HEAVY GAUGE AND AS SHORT AND DIRECT AS POSSIBLE.
- 4. A PAIR OF JT-11P-1 TRANSFORMERS ASSEMBLED AS ABOVE IN A STURDY STEEL BOX WITH GOLD PLATED XLR CONNECTORS AND GROUND LIFT SWITCHES IS AVAILABLE FROM JENSEN AS ISO-MAX® MODEL PI-2XX.

jensen AS089

7135 HAYVENHURST AVE. VAN NUYS, CALIFORNIA 91406 (818) 374-5857

© COPYRIGHT 1993, 1995 JENSEN TRANSFORMERS, INC.